

Truth Table & Minterm Expansion

Computer Science 111
Boston University

Vahid Azadeh-Ranjbar, Ph.D.


Constructive Proof!

- ① Specify a **truth table** defining **any** function you want
- ② For each input row whose output needs to be 1, build an **AND** circuit that outputs 1


input	
x	y
0	0
0	1
1	0
1	1

But... **ALL** functions are just boolean functions: because everything is in binary!

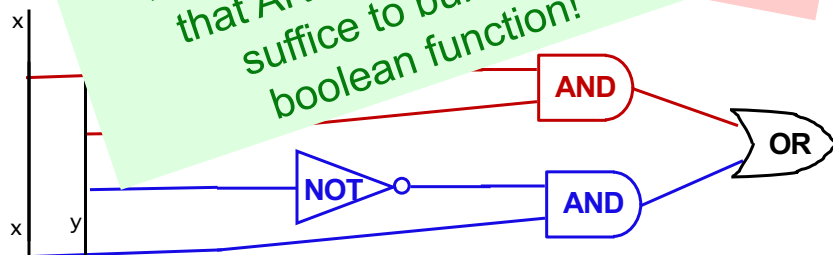This is a constructive proof that AND, OR, and NOT suffice to build any boolean function!



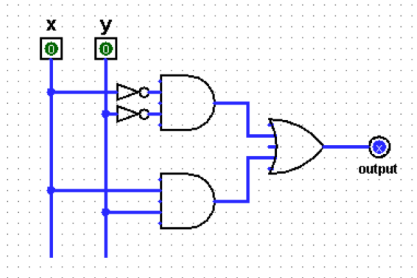
Revisiting the Circuit from Last Class ...



inputs		output
X	Y	
0	0	1
0	1	0
1	0	0
1	1	1

- The top AND gate implements which row of the truth table?
the top row
- The bottom AND gate implements which row?
the bottom row

Boolean Expressions for Truth Tables

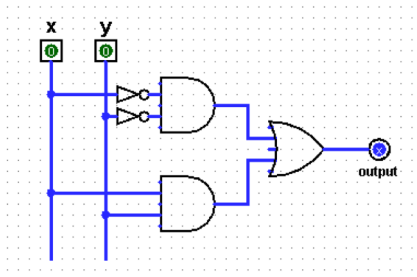

inputs		output
X	Y	
0	0	1
0	1	0
1	0	0
1	1	1

- This truth table/circuit can be summarized by the expression:

$$\bar{x}\bar{y} + xy$$

- This expression is the *minterm expansion* of this truth table.
 - one *minterm* for each row that has an output of 1
 - combined using OR

Building a Minterm Expansion for a Boolean Function

1. If you don't have it, create the truth table.
2. Delete the rows with an output of 0.
3. Create a minterm for each remaining row (the ones with an output of 1):
 - AND the input variables together
 - if a variable has a 0 in that row, negate it
 - example: minterm for the 2nd row
 $\bar{x}\bar{y}z$
4. OR the minterms together.

inputs			output
X	Y	Z	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$$\bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

Minterm Expansion → Circuit

minterm expansion =

$$\bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

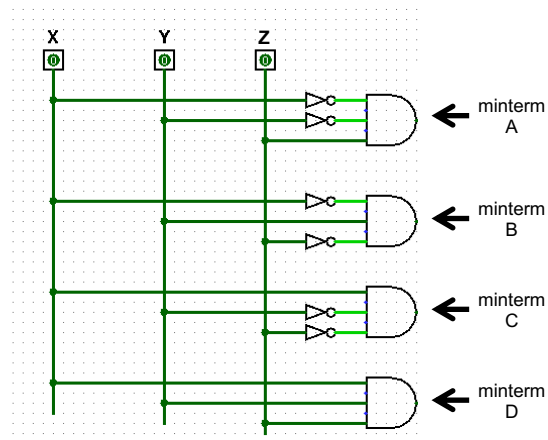\nwarrow minterm A \nwarrow minterm B \nwarrow minterm C \nwarrow minterm D




Minterm Expansion → Circuit

minterm expansion =


$$\bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz$$

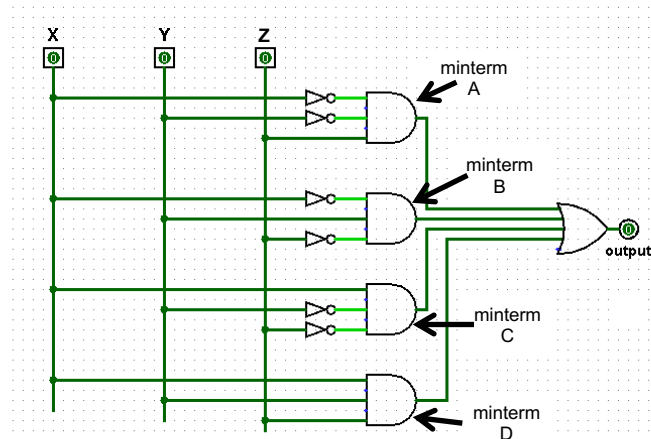\nwarrow minterm A \nwarrow minterm B \nwarrow minterm C \nwarrow minterm D



Odd Parity

inputs			output
X	Y	Z	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

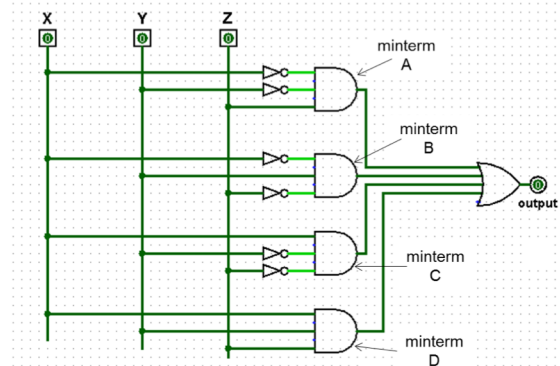

- This truth table and circuit are for the *odd parity* function.
 - outputs 1 when the number of 1 inputs is odd

What is the minterm expansion of this truth table?

inputs			output
x	y	z	
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- A. $yz + xz + xy$
- B. $xyz + x\bar{y}\bar{z} + \bar{x}y\bar{z} + \bar{x}\bar{y}z$
- C. $\bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$
- D. $\bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}z + \bar{x}\bar{y}z$
- E. none of the above

What is the minterm expansion of this truth table?

inputs			output
x	y	z	
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$\bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}z + \textcolor{blue}{x}\textcolor{red}{y}\bar{z}$$

- A. $yz + xz + xy$
- B. $xyz + x\bar{y}\bar{z} + \bar{x}y\bar{z} + \bar{x}\bar{y}z$
- C. $\bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$
- D. $\bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}z + \bar{x}\bar{y}z$
- E. $\textcolor{blue}{none of the above}$

Building a Minterm Expansion for a Boolean Function

ex: greater_than_4(x, y, z)

- 1 if the 3-digit binary number xyz > 4
- 0 otherwise

for example:

- greater_than_4(1, 1, 0) → 1 (True)
because $110_2 = 6_{10}$, and $6 > 4$
- greater_than_4(0, 1, 1) → 0 (False)
because $011_2 = 3_{10}$, and 3 is *not* > 4

Building a Minterm Expansion for a Boolean Function

ex: greater_than_4(x, y, z)

- 1 if the 3-digit binary number xyz > 4
- 0 otherwise

1. If you don't have it, create the truth table.

	inputs			output
<u>dec</u>	<u>x</u>	<u>y</u>	<u>z</u>	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

Building a Minterm Expansion for a Boolean Function

ex: greater_than_4(x, y, z)

→ 1 if the 3-digit binary number xyz > 4
→ 0 otherwise

1. If you don't have it, create the truth table.
2. Delete the rows with an output of 0.

	inputs			output
	x	y	z	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

Building a Minterm Expansion for a Boolean Function

ex: greater_than_4(x, y, z)

→ 1 if the 3-digit binary number xyz > 4
→ 0 otherwise

1. If you don't have it, create the truth table.
2. Delete the rows with an output of 0.
3. Create a minterm for each remaining row (the ones with an output of 1).

	inputs			output
	x	y	z	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

What Is the Minterm for the **BLUE** Row?

<u>dec</u>	<u>inputs</u>			<u>output</u>
	<u>x</u>	<u>y</u>	<u>z</u>	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

- A. $x + \bar{y} + z$
- B. $\bar{x} + y + \bar{z}$
- C. $\bar{x}y\bar{z}$
- D. $x\bar{y}z$
- E. none of the above

What Is the Minterm for the **BLUE** Row?

<u>dec</u>	<u>inputs</u>			<u>output</u>
	<u>x</u>	<u>y</u>	<u>z</u>	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

- A. $x + \bar{y} + z$
- B. $\bar{x} + y + \bar{z}$
- C. $\bar{x}y\bar{z}$
- D. $x\bar{y}z$
- E. none of the above

Building a Minterm Expansion for a Boolean Function

ex: greater_than_4(x, y, z)

→ 1 if the 3-digit binary number xyz > 4
→ 0 otherwise

1. If you don't have it, create the truth table.
2. Delete the rows with an output of 0.
3. Create a minterm for each remaining row (the ones with an output of 1):
 - AND the input variables together
 - if a variable has a 0 in that row, negate it

	inputs			output
<u>dec</u>	<u>x</u>	<u>y</u>	<u>z</u>	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

$x\bar{y}z$ $xy\bar{z}$ xyz

Building a Minterm Expansion for a Boolean Function

ex: greater_than_4(x, y, z)

→ 1 if the 3-digit binary number xyz > 4
→ 0 otherwise

1. If you don't have it, create the truth table.
2. Delete the rows with an output of 0.
3. Create a minterm for each remaining row (the ones with an output of 1):
 - AND the input variables together
 - if a variable has a 0 in that row, negate it
4. OR the minterms together.


	inputs			output
<u>dec</u>	<u>x</u>	<u>y</u>	<u>z</u>	
0:	0	0	0	0
1:	0	0	1	0
2:	0	1	0	0
3:	0	1	1	0
4:	1	0	0	0
5:	1	0	1	1
6:	1	1	0	1
7:	1	1	1	1

$x\bar{y}z + xy\bar{z} + xyz$

Minterm Expansion → Circuit

minterm expansion =

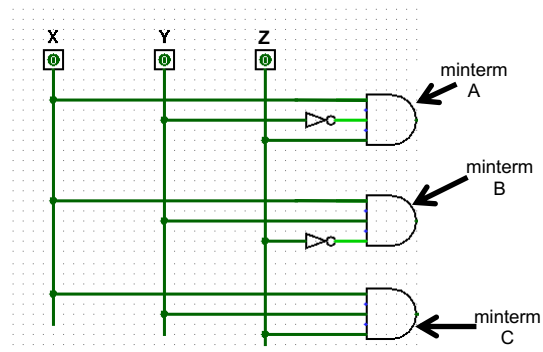
$$\begin{array}{ccc} x\bar{y}z & + & xy\bar{z} & + & xyz \\ \nwarrow & & \nearrow & & \nearrow \\ \text{minterm} & & \text{minterm} & & \text{minterm} \\ \text{A} & & \text{B} & & \text{C} \end{array}$$




Minterm Expansion → Circuit

minterm expansion =
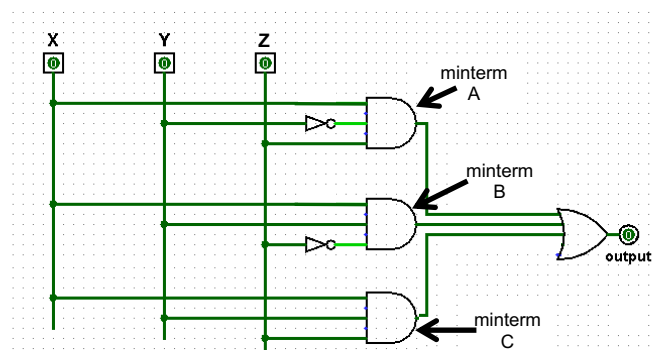
$$\begin{array}{ccc} x\bar{y}z & + & xy\bar{z} & + & xyz \\ \nwarrow & & \nearrow & & \nearrow \\ \text{minterm} & & \text{minterm} & & \text{minterm} \\ \text{A} & & \text{B} & & \text{C} \end{array}$$




Adding "Rails" for the NOT of Each Input

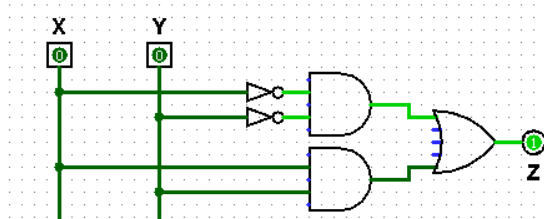

Here's a circuit that we looked at earlier.

It tests whether $x == y$.

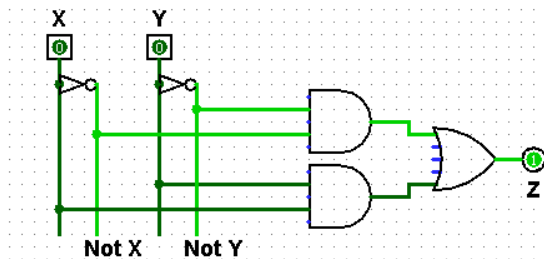


Here's an alternative version that adds "rails" for Not X and Not Y.

In some cases (but not this one!), doing so can reduce the number of NOT gates.


Which AND gate corresponds to row 3 of the table?

	input			output ↓
	x	y	z	
row 0	0	0	0	
row 1	0	0	1	
row 2	0	1	0	
row 3	0	1	1	
row 4	1	0	0	
row 5	1	0	1	
row 6	1	1	0	
row 7	1	1	1	

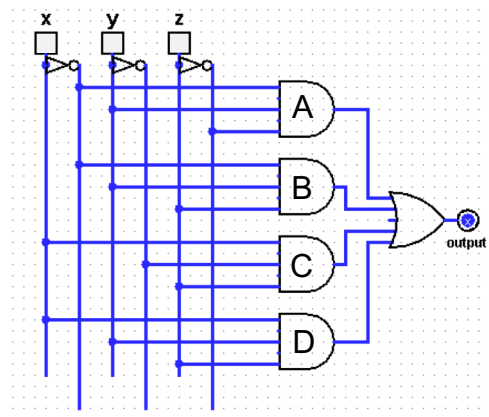

Which AND gate corresponds to row 3 of the table?


	input			output
	x	y	z	
row 0	0	0	0	0
row 1	0	0	1	0
row 2	0	1	0	1
row 3	0	1	1	1
row 4	1	0	0	0
row 5	1	0	1	1
row 6	1	1	0	0
row 7	1	1	1	1

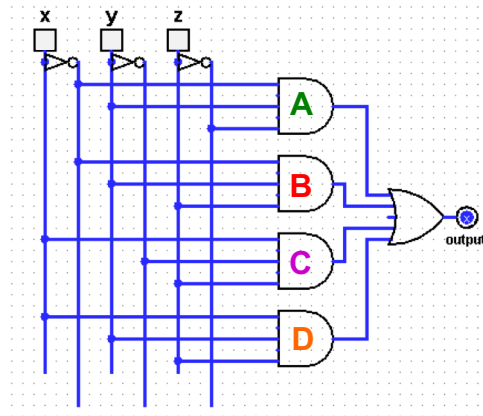

- Complete the rest of the truth table.
- What is its minterm expansion as a formula/expression?
- If the inputs represent a three-bit integer, what property of integers does the circuit compute?

Which AND gate corresponds to row 3 of the table?


	input			output
	x	y	z	
row 0	0	0	0	0
row 1	0	0	1	0
row 2	0	1	0	1
row 3	0	1	1	1
row 4	1	0	0	0
row 5	1	0	1	1
row 6	1	1	0	0
row 7	1	1	1	1

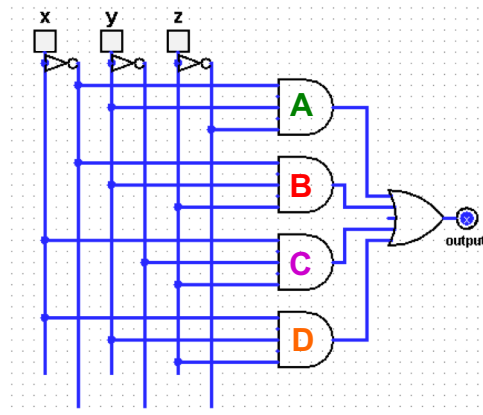

- Complete the rest of the truth table.
- What is its minterm expansion as a formula/expression?
 $\bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z + xyz$
- If the inputs represent a three-bit integer, what property of integers does the circuit compute?


Which AND gate corresponds to row 3 of the table?

	input			output
	x	y	z	
row 0	0	0	0	0
row 1	0	0	1	0
row 2	0	1	0	1
row 3	0	1	1	1
row 4	1	0	0	0
row 5	1	0	1	1
row 6	1	1	0	0
row 7	1	1	1	1

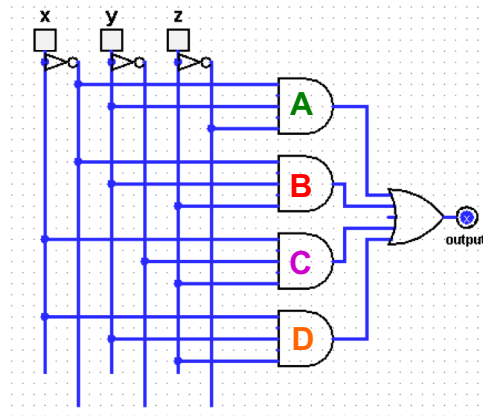


- Complete the rest of the truth table.
- What is its minterm expansion as a formula/expression?
 $\bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z + xyz$
- If the inputs represent a three-bit integer, what property of integers does the circuit compute? *whether the integer is prime*

DIY!

input			output
x	y	z	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

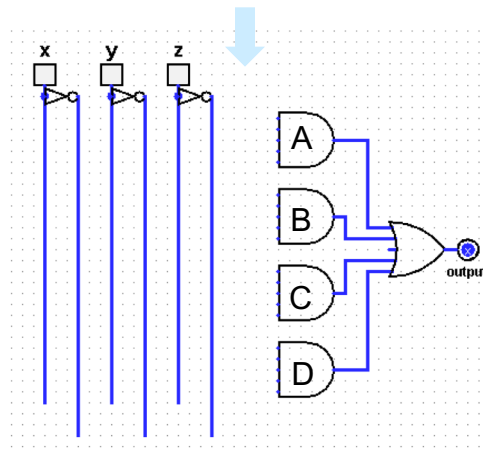Add the wires needed to build a circuit for the truth table at left...




First make a minterm expansion!
Then complete the circuit!

DIY!

input			output
x	y	z	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

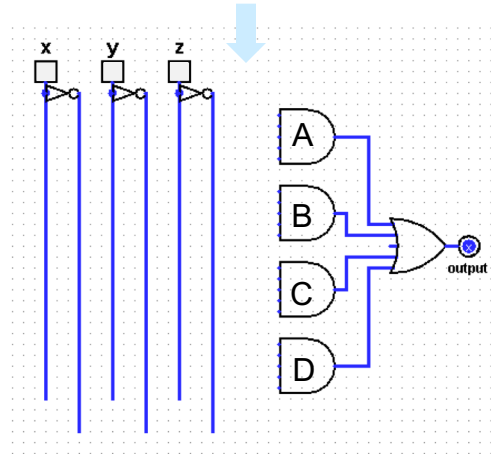Add the wires needed to build a circuit for the truth table at left...




$$\bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$$

DIY!

input			output
x	y	z	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

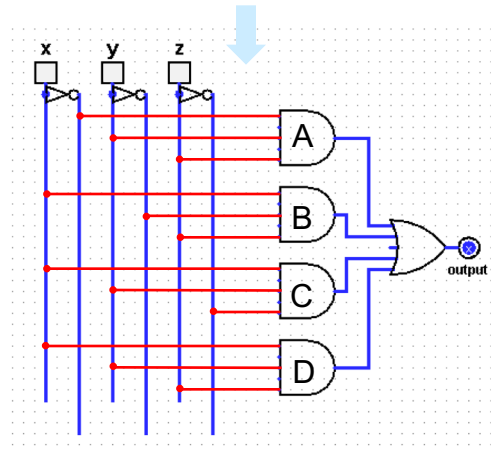Add the wires needed to build a circuit for the truth table at left...




$$\bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$$

DIY!

input			output
x	y	z	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

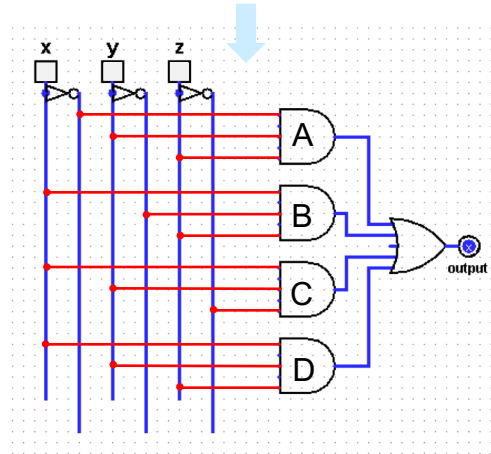Add the wires needed to build a circuit for the truth table at left...




$$\bar{x}y\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$

What does this circuit compute?

DIY!

input			output
x	y	z	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

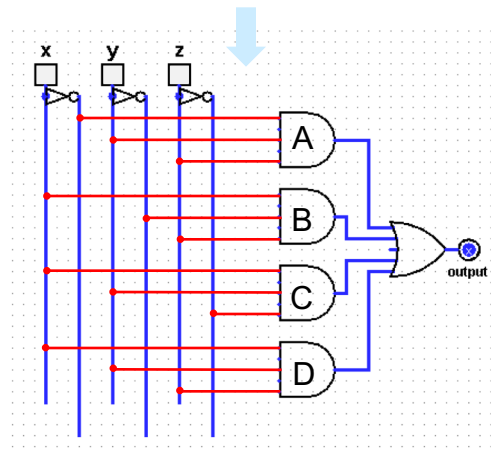Add the wires needed to build a circuit for the truth table at left...





$$\bar{x}y\bar{z} + x\bar{y}z + xy\bar{z} + xyz$$

the majority function – outputs 1 if a majority of the inputs is 1

Physical Logic Gates!

A transistor

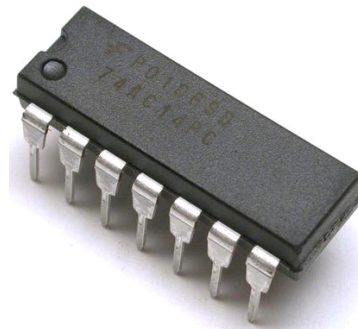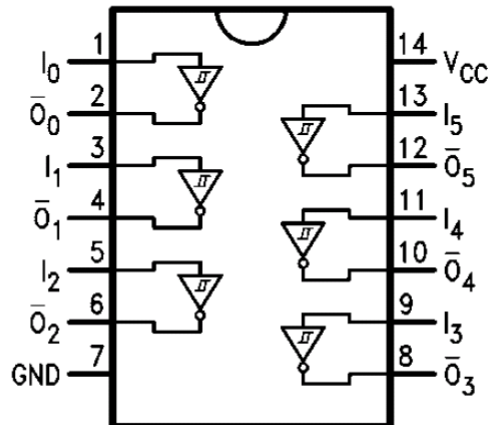

6 NOT gates in one chip!



Advances in the Number of Transistor in IC

MOORE'S LAW "Transistor density on integrated circuits doubles about every two years." *

